

Problem 1

| Write down the potential difference across the capacitor.

$$V_c = \frac{Q}{C}$$
$$V_c(t) = \frac{q(t)}{C}$$

Problem 2

| Write down the potential difference across the resistor.

$$V = -IR$$
$$V_R(t) = I(t)R$$

Problem 3

| Write down the voltage required to overcome the back e.m.f. $V_L(t)$ in the inductance (L).

$$V_L(t) = -L \frac{dI}{dt}$$

Problem 4

| Show that

$$L \frac{dI}{dt} + RI + \frac{q}{C} = 0$$

When the switch is in the right position, we can just use Kirchoff's loop rule for the single loop.

$$\frac{q(t)}{C} - (-I(t)R) - (-L \frac{dI}{dt}) = 0$$

$$L \frac{dI}{dt} + I(t)R + \frac{q(t)}{C} = 0$$

$$L \frac{dI}{dt} + RI + \frac{q}{C} = 0$$

Problem 5

| Show that blank

$$L \frac{dI}{dt} + RI + \frac{q}{C} = 0$$

$$\frac{dI}{dt} + \frac{R}{L}I + \frac{q}{LC} = 0$$

$$2k = \frac{R}{L}$$

$$\omega^2 = \frac{1}{LC}$$

$$\frac{dI}{dt} + 2kI + \omega^2 q = 0$$

$$I = \frac{dq}{dt}$$

$$\frac{d^2q}{dt^2} + 2k \frac{dq}{dt} + \omega^2 q = 0$$

Problem 6

| Using the trivial(?) solution $q = Qe^{\alpha t}$, solve for α .

$$\begin{aligned} q &= Qe^{\alpha t} \\ \frac{dq}{dt} &= \alpha Qe^{\alpha t} \\ \frac{d^2q}{dt^2} &= \alpha^2 Qe^{\alpha t} \end{aligned}$$

$$\begin{aligned} \alpha^2 Qe^{\alpha t} + 2k\alpha Qe^{\alpha t} + \omega^2 Qe^{\alpha t} &= 0 \\ Qe^{\alpha t} (\alpha^2 + 2k\alpha + \omega^2) &= 0 \end{aligned}$$

Solve quadratic

$$\alpha = \frac{-2k \pm \sqrt{4k^2 - 4\omega^2}}{2}$$

Problem 7

| Derive the equation for R that determines the onset of critical damping.

Zooming in on that quadratic, $\sqrt{4k^2 - 4\omega^2}$ must be 0.

$$\begin{aligned} 4k^2 - 4\omega^2 &= 0 \\ k^2 &= \omega^2 \\ \frac{R^2}{L^2} &= \frac{1}{LC} \\ \frac{R^2}{L} &= \frac{1}{C} \\ R^2 &= \sqrt{\frac{L}{C}} \end{aligned}$$

Problem 8

| For $L=0.50$ H and $C=1.80e-9$ F, what is the maximum value for resistance so that the circuit is underdamped.

$\sqrt{4k^2 - 4\omega^2}$ must be < 0 .

$$\begin{aligned} k^2 - \omega^2 &< 0 \\ R^2 &< \sqrt{\frac{L}{C}} \\ R^2 &< \sqrt{\frac{0.50}{1.8\mu F}} \end{aligned}$$

R must be less than 527 Ω

Problem 9

| If the resistance in an underdamped LRC oscillator is decreased by a factor of two, from $R = 2R_0$ to $R = R_0$, how much does the oscillation amplitude change over a time $t = 2L/R_0$?

General solution is

$$y = e^{\gamma t} [C_1 \cos(\beta t) + C_2 \sin(\beta t)]$$

Solution to characteristic equation

$$\begin{aligned} r &= \gamma \pm \beta i \\ \alpha &= -k \pm \sqrt{k^2 - \omega^2} \\ \sqrt{k^2 - \omega^2} &= \beta i \end{aligned}$$

$$\gamma = -k$$

$$y = e^{-kt} [C_1 \cos(\beta t) + C_2 \sin(\beta t)]$$

$$y = e^{-\frac{R}{2L}t}$$

Problem 10

If the resistance in an underdamped LRC oscillator is decreased by a factor of two, from $R = 2R_0$ to $R = R_0$, how much does the oscillation amplitude change over a time $t = 2L/R_0$?

General solution is

$$y = e^{\gamma t} [C_1 \cos(\beta t) + C_2 \sin(\beta t)]$$

Solution to characteristic equation

$$r = \gamma \pm \beta i$$

$$\alpha = -k \pm \sqrt{k^2 - \omega^2}$$

$$\sqrt{k^2 - \omega^2} = \beta i$$

$$\gamma = -k$$

$$y = e^{-kt} [C_1 \cos(\beta t) + C_2 \sin(\beta t)]$$

$$y = e^{-\frac{R}{2L}t}$$

$$R = 2R_0 \rightarrow y = e^{-\frac{2R_0}{2L}t} = e^{-\frac{2R_0}{2L} \frac{2L}{R_0}} = e^{-2} A$$

$$R = R_0 \rightarrow y = e^{-\frac{R_0}{2L}t} = e^{-\frac{R_0}{2L} \frac{2L}{R_0}} = e^{-1} A$$

Oscillation amplitude decreases by a factor of $1/e$

Problem 11

Discuss how the “beating” effect in a coupled oscillator system is different than the beating of acoustic waves.

In the case of acoustic waves interacting to create a beat, we’re just talking about two waves summing constructively and destructively. In the case of CEO, the coupled oscillator system is not described by the addition of two constant waves, but rather by a second order differential equation. Rather than two waves being created by entirely different sources, in CEO the capacitor and inductors are actually causing time delays in the flow of current as it flows around the circuit and is slowly dissipated by the resistor. If the system were not operating in a normal mode, these “beats” would not be apparent.