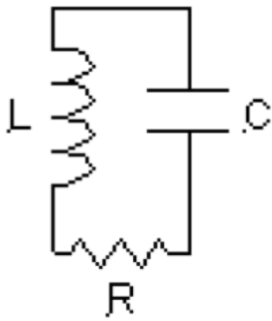


## Appendix A: LRC Electrical Harmonic Oscillator Equation Derivation



Kirchoff's Voltage Rule:  $\sum_{loop} V = 0$

Voltages across capacitor, resistor, and inductor:

$$V_C - V_R - V_L = 0$$

Substitute:

$$\frac{q}{C} + IR - \left(-L \frac{dI}{dt}\right) = 0$$

Rearrange:

$$L \frac{dI}{dt} + IR + \frac{q}{C} = 0$$

Divide by L:

$$\frac{dI}{dt} + \frac{R}{L} I + \frac{1}{LC} q = 0$$

Substitute:  $I = \frac{dq}{dt}$  and  $\frac{dI}{dt} = \frac{d^2q}{dt^2}$

$$\frac{d^2q}{dt^2} + \left(\frac{R}{L}\right) \frac{dq}{dt} + \frac{1}{LC} q = 0$$

Say  $\frac{R}{L} = \gamma$ ,  $\frac{1}{LC} = \omega_0^2$ :

$$\frac{d^2q}{dt^2} + \gamma \frac{dq}{dt} + \omega_0^2 q = 0$$

↳ Second order differential equation

Propose solution  $q(t) = q_0 e^{rt}$

$$\frac{dq(t)}{dt} = r q_0 e^{rt}, \quad \frac{d^2q(t)}{dt^2} = r^2 q_0 e^{rt}$$

Plug in to diff eq:

$$q_0 r^2 e^{rt} + q_0 r e^{rt} \gamma + \omega_0^2 q_0 e^{rt} = 0$$

Simplify:

$$q_0 e^{rt} (r^2 + \gamma r + \omega_0^2) = 0$$

Characteristic equation

Make true by solving characteristic eqn with quadratic formula:

$$r = \frac{-\gamma \pm \sqrt{\gamma^2 - 4\omega_0^2}}{2}$$


For underdamped,

$$r = \gamma \pm i\omega_0 i$$

From Euler's Formula

$$q(t) = q_0 e^{\left(-\frac{\gamma t}{2}\right)} \cos(\omega_0 t)$$
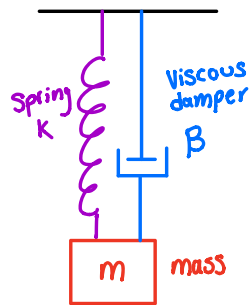
## Appendix B: Damped Hanging Mass Spring Oscillator Equation Derivation



Force Balance of damper and spring force

$$ma = -bv + Kx$$

Write derivatives and rearrange:

$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + Kx = 0$$

divide by  $m$ :

$$\frac{d^2x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{K}{m} x = 0$$

Say  $\gamma = \frac{b}{m}$  and  $\omega_0 = \frac{K}{m}$ :

$$\frac{d^2x}{dt^2} + \gamma \frac{dx}{dt} + \omega_0^2 x = 0$$

↳ second order differential equation

Propose solution  $x(t) = x_0 e^{rt}$

$$\frac{dx(t)}{dt} = x_0 r e^{rt}, \quad \frac{d^2x(t)}{dt^2} = x_0 r^2 e^{rt}$$

Plug in to diff eq:

$$x_0 r^2 e^{rt} + x_0 r e^{rt} \gamma + \omega_0^2 x_0 e^{rt} = 0$$

Simplify:

$$x_0 e^{rt} (r^2 + \gamma r + \omega_0^2) = 0$$

Characteristic equation

make true by solving characteristic eqn with quadratic formula:

$$r = \frac{-\gamma \pm \sqrt{\gamma^2 - 4\omega_0^2}}{2}$$


For underdamped,

$$r = \gamma \pm i\omega_d$$

From Euler's Formula

$$x(t) = x_0 e^{-\frac{\gamma t}{2}} \cos(\omega_d t)$$
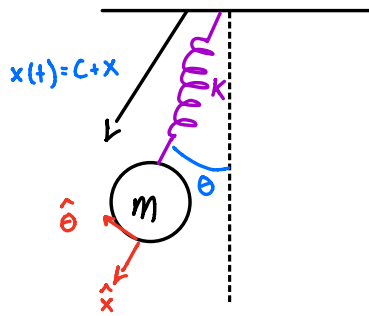
## Appendix C: Equations of Motion of Elastic Pendulum Derivation



Total Kinetic Energy

$$T = \frac{1}{2} m (\dot{v}_r^2 + \dot{v}_\theta^2) = \frac{1}{2} m (\dot{x}^2 + (x(t)\dot{\theta})^2) = \frac{1}{2} m (\dot{x}^2 + (C+x)^2 \dot{\theta}^2)$$

Total Potential Energy

$$U = \frac{1}{2} k x^2 - mg(C+x)\cos\theta$$

Define Lagrangian:

$$\mathcal{L} = T - U = \frac{1}{2} m \dot{x}^2 + \frac{1}{2} m (C+x)^2 \dot{\theta}^2 + mg(C+x)\cos\theta - \frac{1}{2} k x^2$$

x equation:  $\frac{\partial}{\partial t} \left( \frac{\partial \mathcal{L}}{\partial \dot{x}} \right) = \frac{\partial \mathcal{L}}{\partial x}$

$$m\ddot{x} - (m(C+x)\dot{\theta}^2 + mg\cos\theta - kx) = 0$$


$$\cancel{m}\ddot{x} - \cancel{m}(C+x)\dot{\theta}^2 + \frac{kx}{\cancel{m}} - \cancel{m}g\cos\theta = 0$$

theta equation:  $2\cancel{m}(C+x)\dot{x}\dot{\theta} + \cancel{m}(C+x)^2\ddot{\theta} + \cancel{m}g(C+x)\sin\theta = 0$

$$\ddot{x} = (C+x)\dot{\theta}^2 - \frac{k}{m}x + g\cos\theta$$

$$\ddot{\theta} = -\frac{2}{C+x}\dot{x}\dot{\theta} - \frac{g}{C+x}\sin\theta$$
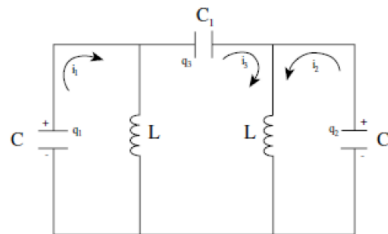
## Appendix D: Coupled LRC Circuit derivation



Coupled LRC circuits  
without resistance

Equations describing circuit from Kirchhoff's Laws:

$$\frac{q_1}{C} = L \frac{d}{dt} (i_1 - i_3)$$

$$\frac{q_2}{C} = L \frac{d}{dt} (i_2 + i_3)$$

$$\frac{q_1}{C} = \frac{q_2}{C} - \frac{q_3}{C_1}, \text{ so } i_3 = \frac{C_1}{C} (i_2 - i_1)$$

Combining above:

$$\frac{q_1}{C} = L \frac{d}{dt} \left[ i_1 \left( 1 + \frac{C_1}{C} \right) - \frac{C_1}{C} i_2 \right]$$

$$\frac{q_2}{C} = L \frac{d}{dt} \left[ i_2 \left( 1 + \frac{C_1}{C} \right) - \frac{C_1}{C} i_1 \right]$$

Take sum and difference of above

$$(q_1 + q_2) \frac{1}{C} = L \frac{d}{dt} (i_1 + i_2)$$

$$(q_1 - q_2) \frac{1}{C} = \frac{1}{C} (C + 2C_1) \frac{d}{dt} (i_1 - i_2)$$

Define  $q_+ = q_1 + q_2$  and  $q_- = q_1 - q_2$  and substitute

$$\frac{d^2}{dt^2} q_+ + \frac{1}{LC} q_+ = 0$$

Second order diff. eq

$$\frac{d^2}{dt^2} q_- + \frac{1}{L(C + 2C_1)} q_- = 0$$

Second order diff. eq

Solve differential equations using methods in above appendices

$$q_+ = q_{+0} \sin(\omega_+ t) \quad q_- = q_{-0} \sin(\omega_- t)$$

$$\text{Where } \omega_+ = \frac{1}{\sqrt{LC}} \quad \text{and} \quad \omega_- = \frac{1}{\sqrt{L(C + 2C_1)}}$$